

Smt. Chandibai Himathmal Mansukhani College

Computer Organization and Design (USCS101)

Practical 1: Digital Electronics (Study of Logic Gates)

Learning Objectives

Students will be able to:

Content:

- How one can derive the Boolean expression from given logic gate
- How to design logic circuit using logisim software
- How to represent the logic gates on circuit diagram

Process:

- How to combine various inputs to achieve desired outputs with the help of logic gates
- Create truth tables from logic gates

Prior Knowledge :

- Recognize high/low, 1/0 as two state logic levels

1. To study the operation and verify the truth table of the basic logic gates such as AND, OR, NOT, NOR, NAND, EX-OR and EX-NOR using logisim

i. AND Gate

Circuit Symbol	Truth table	Boolean Expression															
	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td></tr></table>	A	B	C													
A	B	C															

ii. NOT Gate

Circuit Symbol	Truth table	Boolean Expression						
	<table><tr><th>A</th><th>B</th></tr><tr><td></td><td></td></tr><tr><td></td><td></td></tr></table>	A	B					
A	B							

Smt. Chandibai Himathmal Mansukhani College

iii. OR Gate

Circuit Symbol	Truth table	Boolean Expression															
	<table> <tr> <th>A</th><th>B</th><th>C</th></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> </table>	A	B	C													
A	B	C															

iv. NOR Gate

Circuit Symbol	Truth table	Boolean Expression															
	<table> <tr> <th>A</th><th>B</th><th>C</th></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> </table>	A	B	C													
A	B	C															

v. NAND Gate

Circuit Symbol	Truth table	Boolean Expression															
	<table> <tr> <th>A</th><th>B</th><th>C</th></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> </table>	A	B	C													
A	B	C															

vi. EX-OR Gate

Circuit Symbol	Truth table	Boolean Expression															
	<table> <tr> <th>A</th><th>B</th><th>C</th></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td></tr> </table>	A	B	C													
A	B	C															

vii. EX-NOR Gate

Circuit Symbol	Truth table	Boolean Expression																		
	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>C</th></tr> </thead> <tbody> <tr><td> </td><td> </td><td> </td></tr> <tr><td> </td><td> </td><td> </td></tr> <tr><td> </td><td> </td><td> </td></tr> <tr><td> </td><td> </td><td> </td></tr> <tr><td> </td><td> </td><td> </td></tr> </tbody> </table>	A	B	C																
A	B	C																		

2. Realize the Basic gates with a universal gate (using NAND) by drawing the logic circuit
- a) Implementing NOT using NAND Gate

- b) Implementing AND using NAND Gate

c) Implementing OR using NAND Gate




3. Draw the circuit diagrams to show how a NOR gate can be made into a NOT gate



4. Construct a truth tables for each the following circuit of logic gates and also drive the corresponding Boolean expression for it

i.

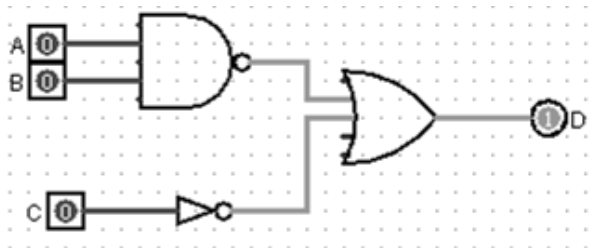


Smt. Chandibai Himathmal Mansukhani College

Expression: _____

Truth Table:

A	B	$(AB)'$	C	C'	$D=(AB)'+C'$

ii.

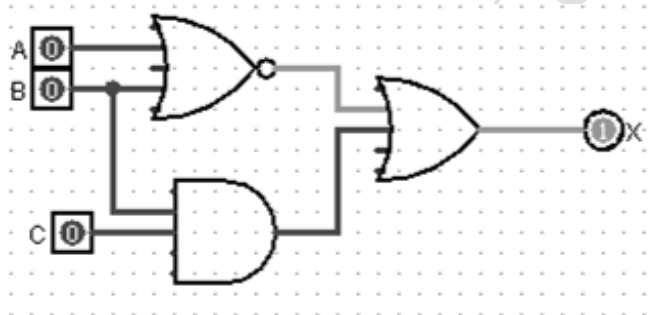

Expression: _____

Truth Table:

A	B	C	A+B	$(A+B)'$	BC	$X=(A+B)'+BC$

Smt. Chandibai Himathmal Mansukhani College

Logic Circuit:



Truth Table:

A	B	C	C'	A+B	(A+B)C'


7. Derive the truth table of AND and OR GATE by taking three inputs and also draw the logic circuit for the same

Truth Table:


A	B	C	AND	OR

Smt. Chandibai Himathmal Mansukhani College

Circuit Diagram for AND Gate:

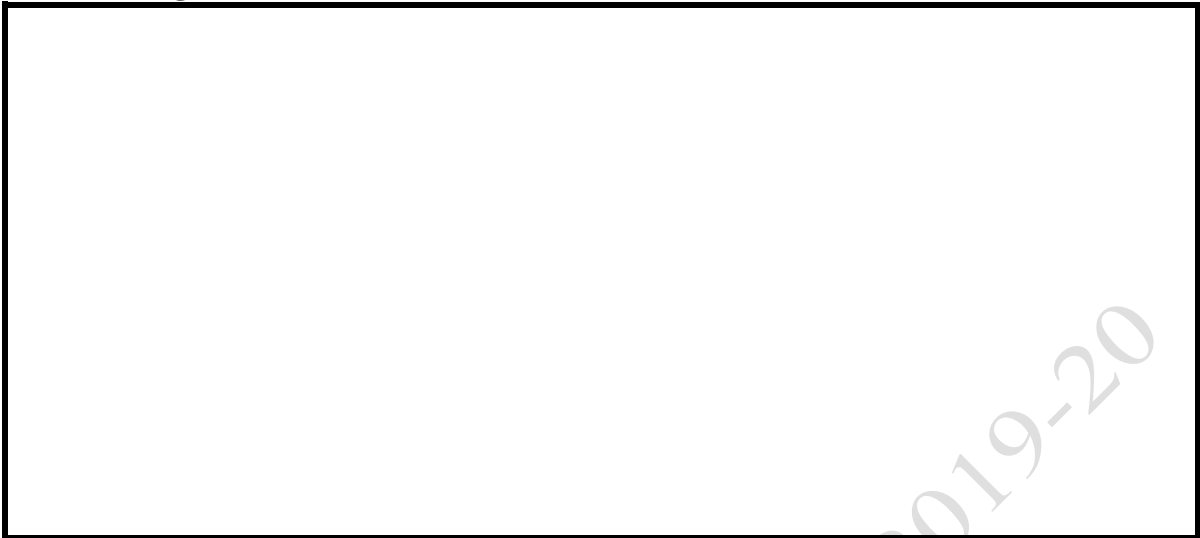

Circuit Diagram for OR Gate:



8. Construct a logic circuit for the Boolean expression for the following:

a. $A.B+C$



Smt. Chandibai Himathmal Mansukhani College

b. $(A.B)' + C.D + (E.F)'$

c. $(X'+Y).(X+Z).(Y+Z)$

Date : _____

Teachers Signature: _____

Batch: _____ / Roll No: _____